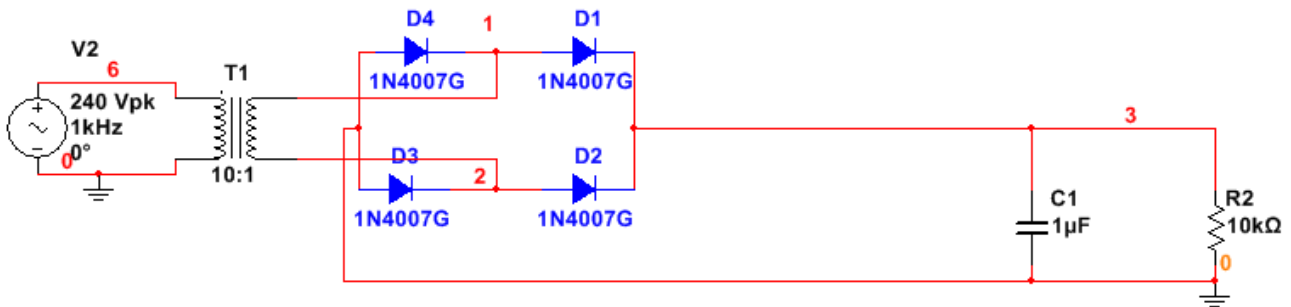



Lab 0

Diodes: Full wave Rectifier

Circuit:




Graph:

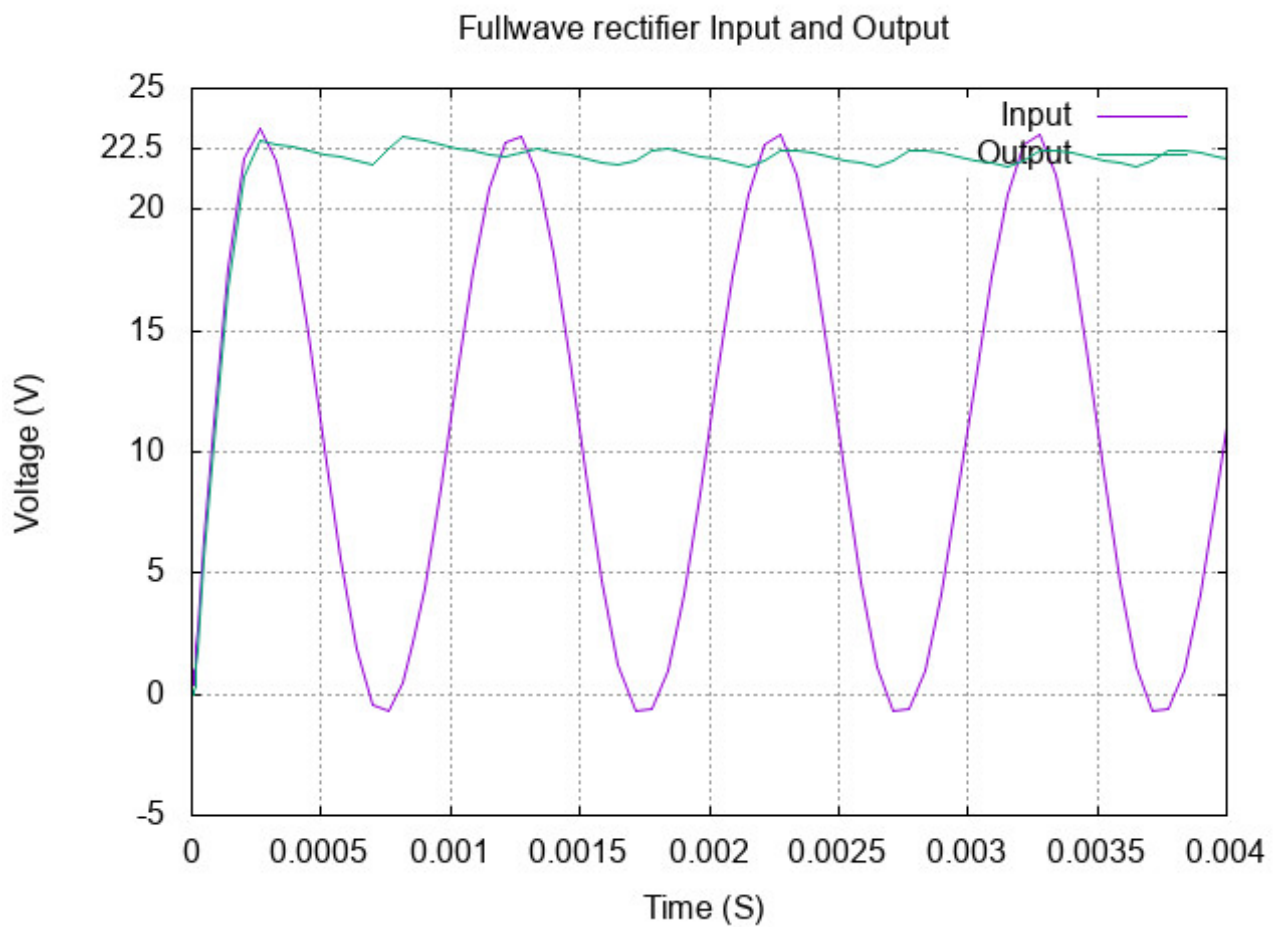


Centre tap transformer

Circuit:

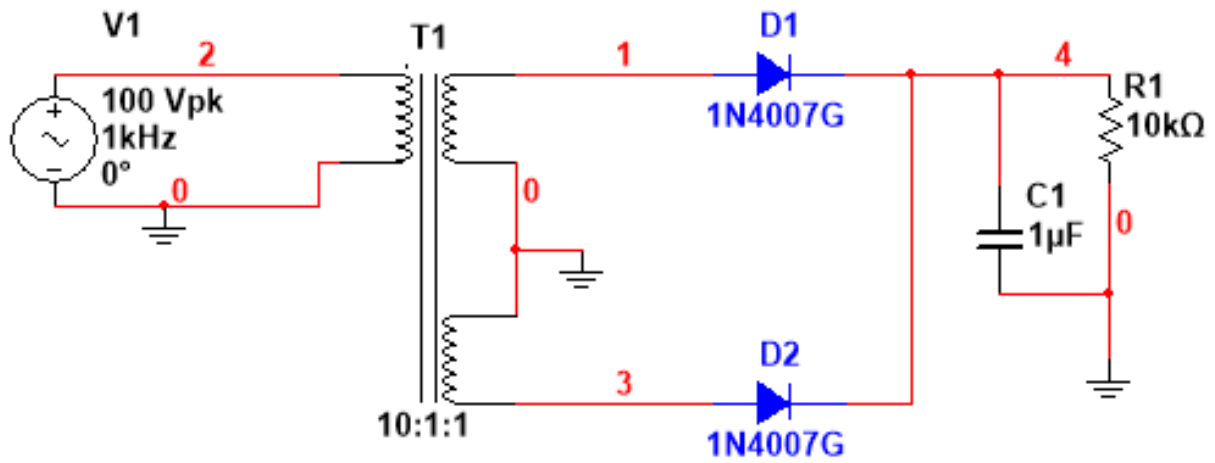


Graph:

Center tap transformer: Input and output

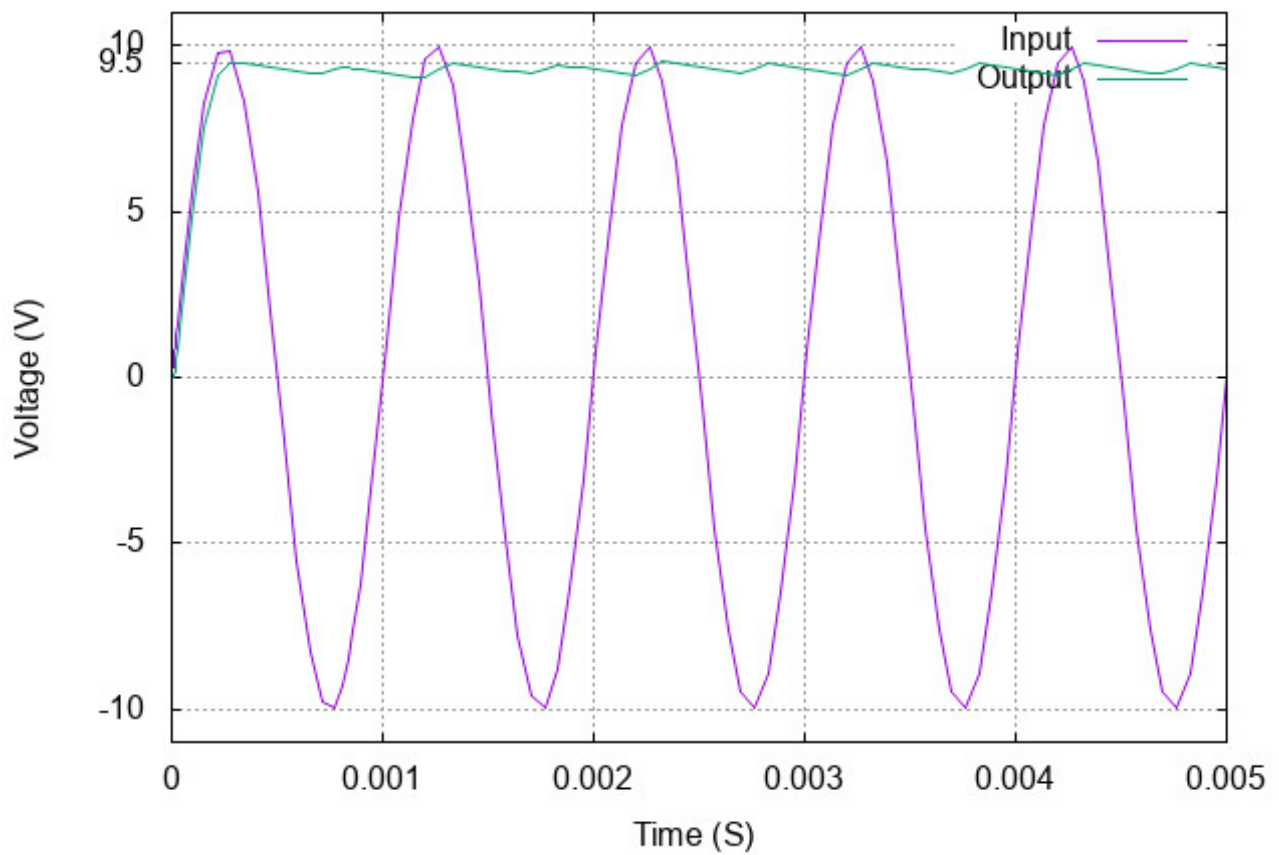


Lab 1

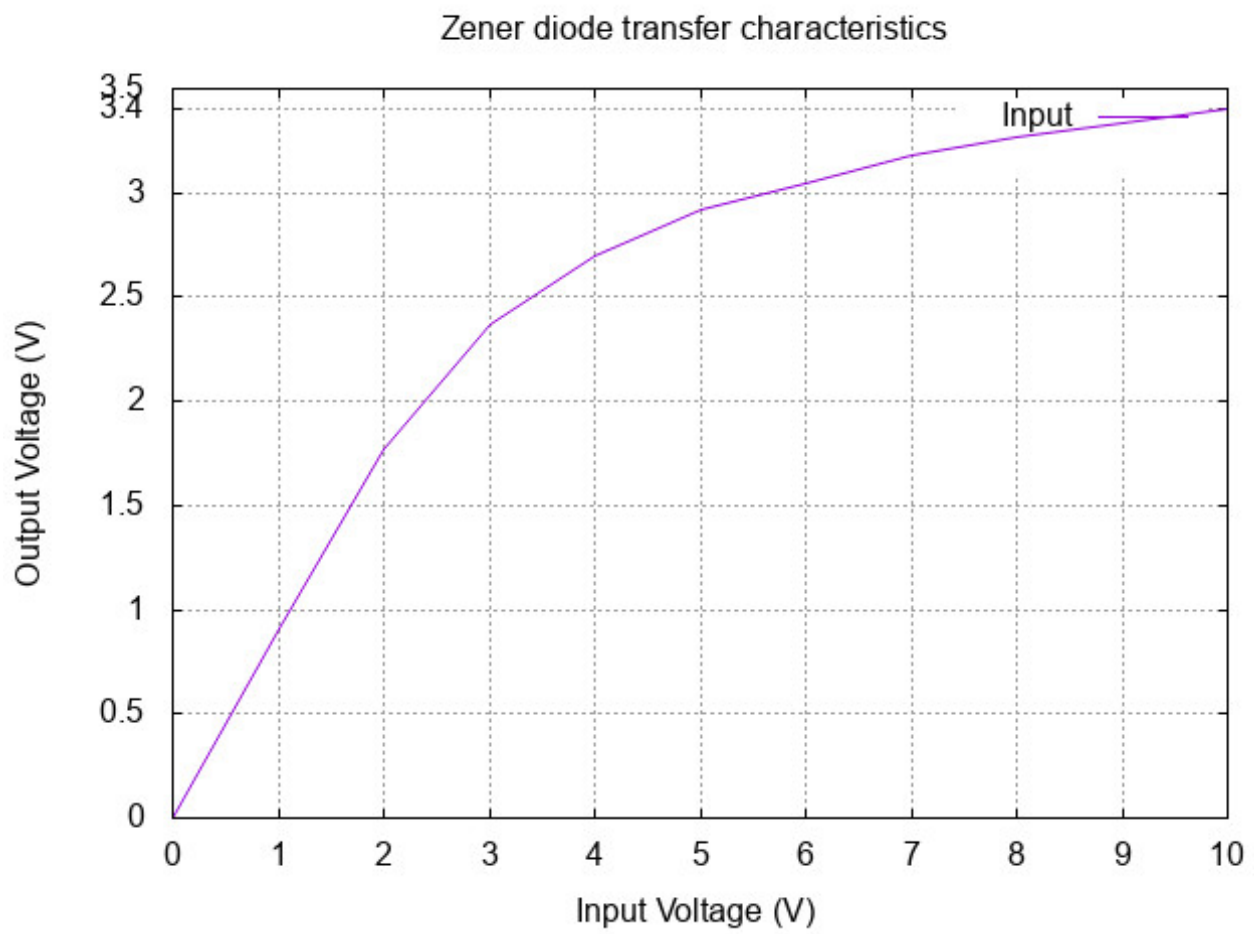Zener Diode Transfer characteristics of output versus input voltage



Zener Diode Bridge Configuration

Circuit

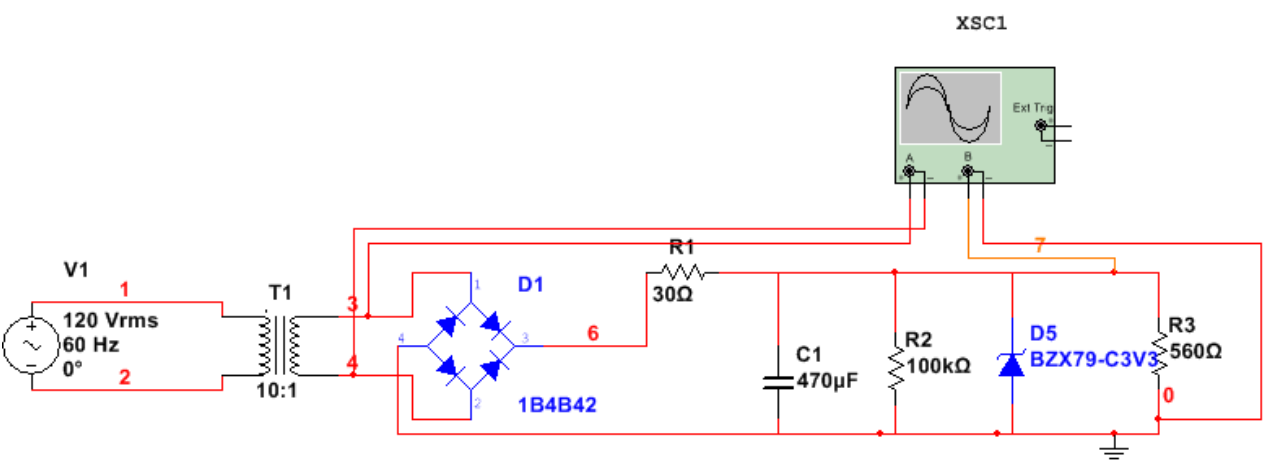

Graph

