
Electronic Devices and Circuits lab

Lab 2 and Lab 3 Consolidated lab report IMT2015524 Aravind Reddy V, IMT2015525 Gnaneswara Reddy YVS


Lab 2


Summing Amplifier

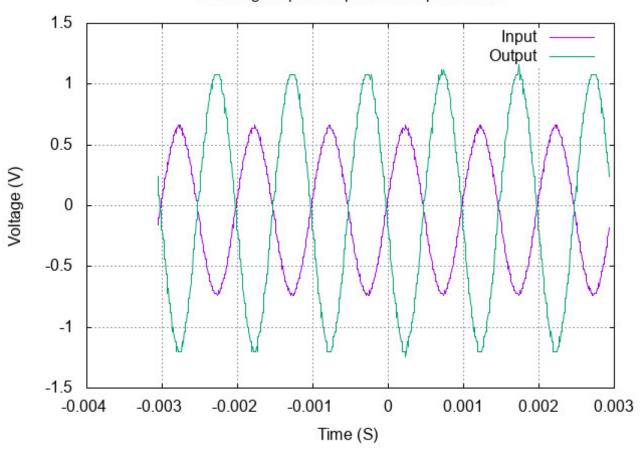Summing Amplfier: input and output vs time




Differentiator

 

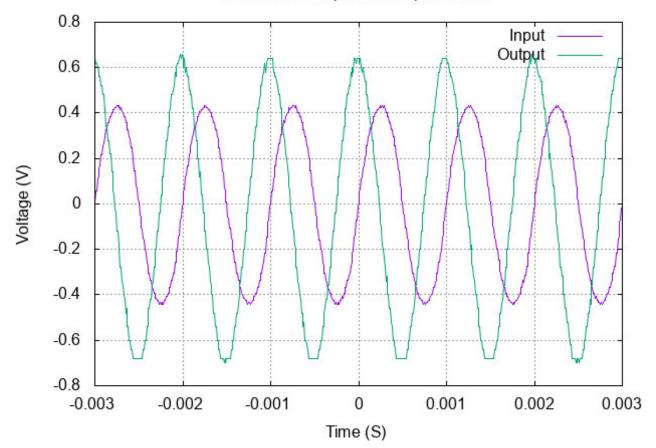

Integrator




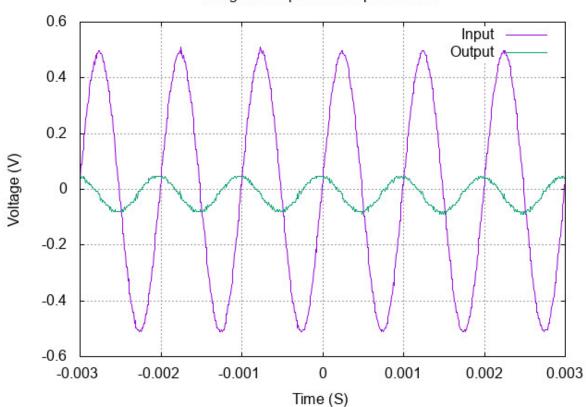


Lab 3


Half Wave Rectifier



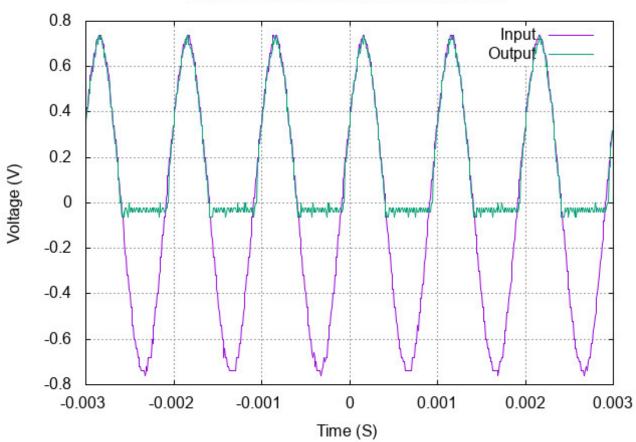

Rectifier

 

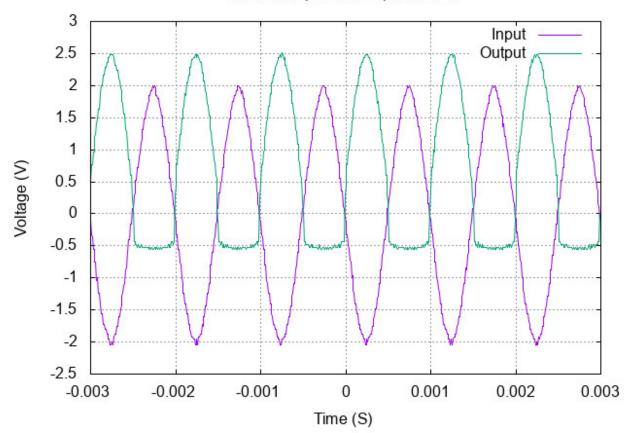

Clamper

