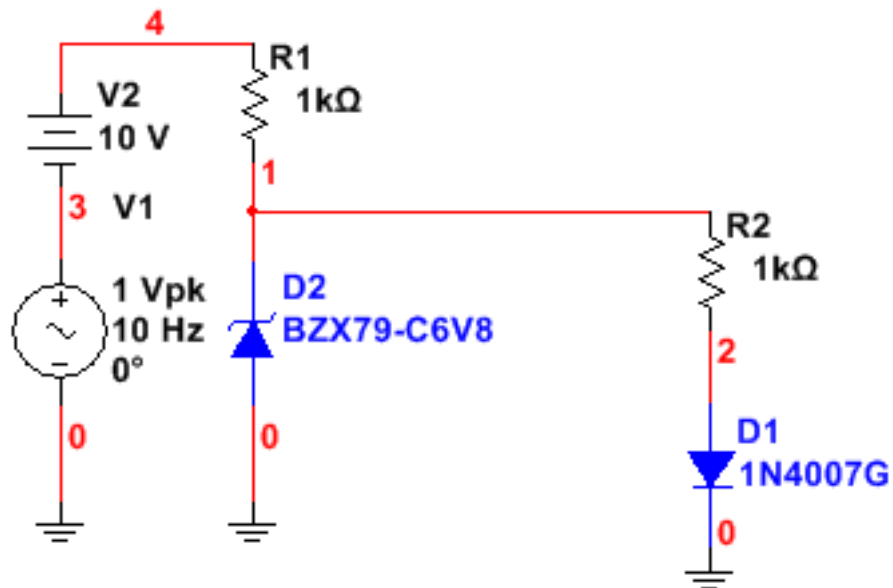


Assignment 0


Group members:

IMT2015516 P Vamshi Krishna
IMT2015524 Aravind Reddy V
IMT2015526 Alan Israel M
IMT2015527 Bharath N
IMT2015528 Prachi Pravin D

Question: Find current at 1 and 2



Output from simulation

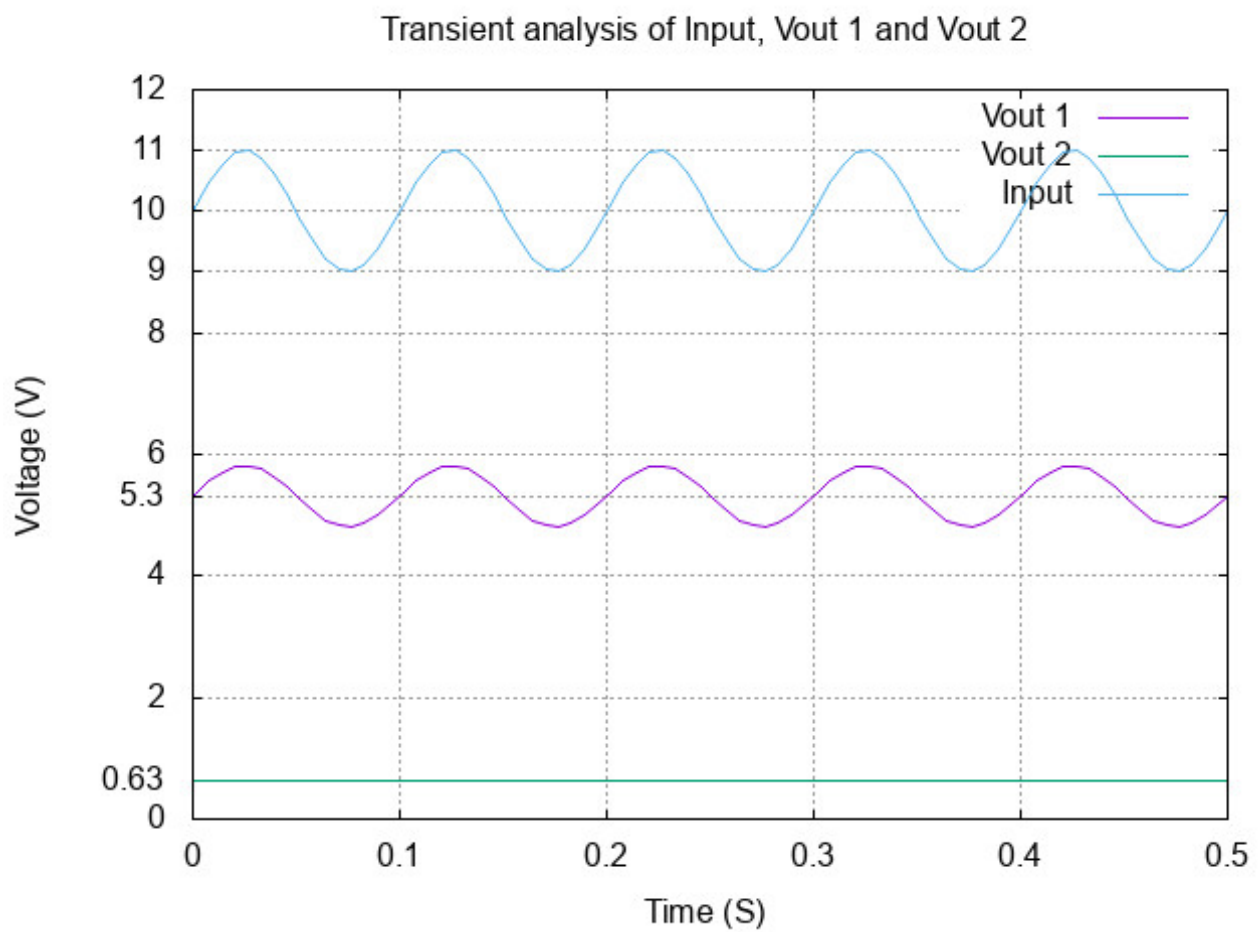

Current at 1 = $(10 - 5.3)/(1 \text{ K Ohm}) = 4.7 \text{ mA}$

As Diode D2 breaks the circuit, current at 2 = current at 1 = 4.7 mA

$$I1 = I2 = 4.7 \text{ mA}$$